



Electric Bell

Construction:

- 1) Electromagnet inside the bell.
- 2) Copper wire wound around an iron piece. This coil acts as an electromagnet.
- 3) Iron strip with striker near the electromagnet.
- 4) Contact screw is in touch with the strip.

Working:

- 1) The current flows through the circuit, when the key is turned on.
- 2) The coil becomes an electromagnet.
- 3) Attracts the iron strip towards it.
- 4) The striker, attached to the iron strip, hits the gong.
- 5) Contact between the iron strip and the contact screw is broken.
- 6) The circuit is broken, the electric current stops.
- 7) The electromagnet stops acting as a magnet.
- 8) The iron strip goes back to its original position.
- 9) contact between the contact screw and the iron strip is restored.
- 10) Current starts flowing again, Electromagnet created.
- 11) Iron strip gets attracted to the magnet again.
- 12) This continues till the plug key is on.

This is how an electric bell works.

